A complete LED circuit

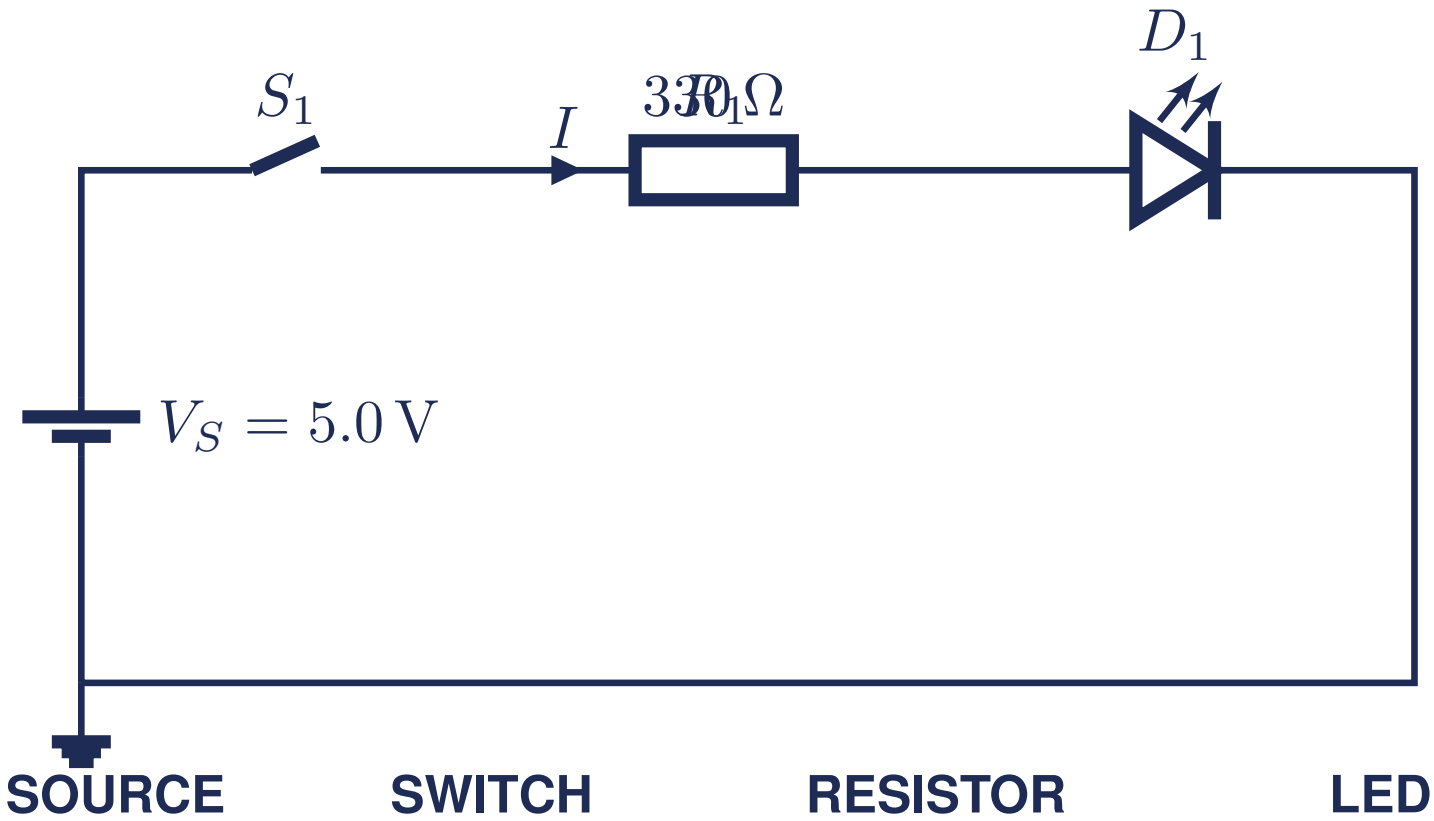

Closing S_1 completes one current path. R_1 limits current through the LED.