LOOP 2 KVL

source rise R_2 drop opposite shared current

$$+6 - 5I_2 + 2(I_1 - I_2) = 0$$

Collect I_1 and I_2 terms

$$\boxed{-2I_1 + 7I_2 = 6}$$