From Two Loops to a Matrix

A guided Kirchhoff and Jupyter bridge

Student number and last name: _____

Class or period: _____

Learning goals

By the end of this bridge, I can:

- define the three current directions in a two-loop circuit;
- write one KVL equation for each loop and handle the shared resistor;
- rearrange both equations into the same variable order;
- build $A\mathbf{x} = \mathbf{b}$ and solve it numerically and symbolically;
- verify the result with KCL, KVL, and a residual.

Why this is useful

Two loops share one component, so the current through that component depends on both loop currents. A matrix does not replace Kirchhoff's laws. It organizes the equations after the circuit reasoning is complete.

What you will make

You will submit one notebook showing this complete chain:

arrows $\longrightarrow$ two KVL equations $\longrightarrow$ standard form $\longrightarrow$ $A\mathbf{x} = \mathbf{b}$ $\longrightarrow$ two solver methods $\longrightarrow$ checks

Before you start

- Use your returned Question 4 work and the released answer for comparison.
- Download the course notebook from the assignment page.
- Keep resistance in $\mathrm{k}\Omega$, voltage in V, and current in mA.
- This checkpoint is a computational verification activity. No physical lab is required.

Textbook support: Grob, Chapter 9, pp. 264–281. **Practice support:** Problems Manual, Chapter 9.
Engagement review: ElectroBOOM101-008: Kirchhoff Circuit Laws.

Start with current directions and the shared branch

1 Define the variables before writing equations

For the completed Question 4 circuit, use clockwise mesh currents I_1 and I_2. The two mesh currents move through the shared resistor in opposite directions. Define I_3 downward through the shared resistor.

$$I_3 = I_1 - I_2$$

This is KCL at the shared branch. It fixes the meaning of every later sign.

I_1	clockwise current assigned to Loop 1
I_2	clockwise current assigned to Loop 2
I_3	downward current through R_3, defined as $I_1 - I_2$

2 Use one sign rule from start to finish

As you walk around a loop:

Source from $-$ to $+$	voltage rise: write $+V_S$
Source from $+$ to $-$	voltage drop: write $-V_S$
Resistor in the current direction	voltage drop: write $-IR$
Resistor against the current direction	voltage rise: write $+IR$


Essential skill: do not jump directly to the matrix. First write the signed KVL terms in the order encountered around each loop. Then substitute $I_3 = I_1 - I_2$.

Quick check before continuing

If the final value of I_3 is negative, what would that mean?

Loop 1: write, substitute, expand, and collect

3 Walk clockwise around Loop 1

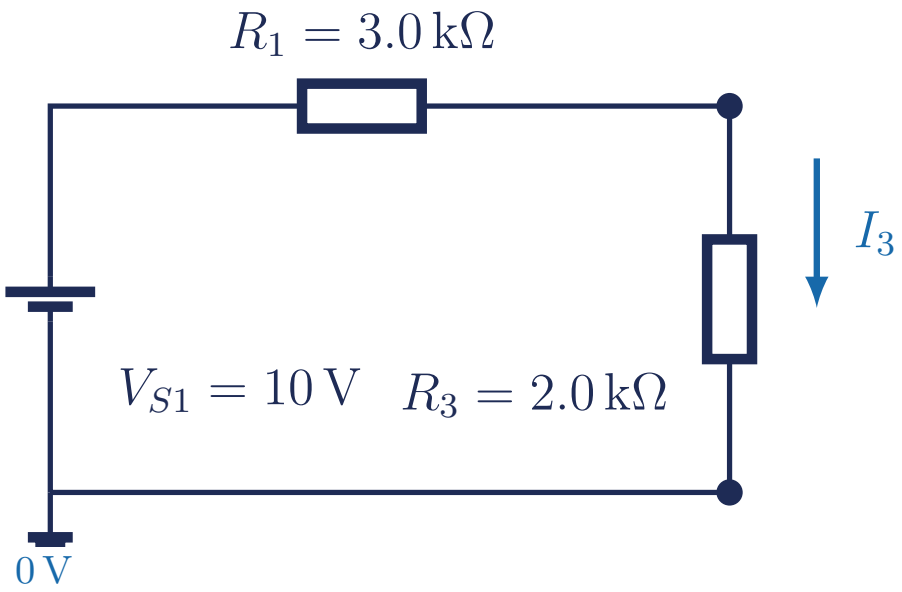

Element	Signed KVL term	Reason
$V_{S1} = 10\,\text{V}$	$+10$	rise through the source
$R_1 = 3.0\,\text{k}\Omega$	$-3I_1$	travel with I_1
$R_3 = 2.0\,\text{k}\Omega$	$-2I_3$	travel with the defined I_3

Write KVL:

$$+10 - 3I_1 - 2I_3 = 0$$

Substitute the shared current:

$$+10 - 3I_1 - 2(I_1 - I_2) = 0$$

Expand the bracket:

$$+10 - 3I_1 - 2I_1 + 2I_2 = 0$$


Collect like terms and move the source to the right:

$$+10 - 5I_1 + 2I_2 = 0 \quad \Longrightarrow \quad \boxed{5I_1 - 2I_2 = 10}$$

The first matrix row is read directly from the standard-form equation: coefficient of I_1, coefficient of I_2, right side. Therefore Row 1 is $[5, -2]$ and $b_1 = 10$.

Loop 2: the shared resistor changes sign

4 Walk clockwise around Loop 2

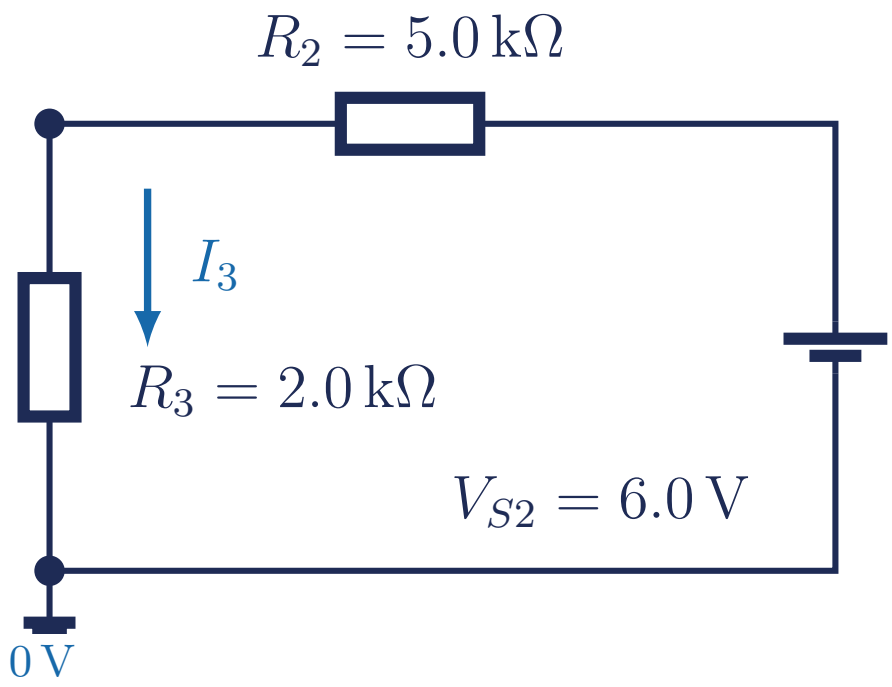

Element	Signed KVL term	Reason
$V_{S2} = 6.0\,\text{V}$	$+6$	rise through the source
$R_2 = 5.0\,\text{k}\Omega$	$-5I_2$	travel with I_2
$R_3 = 2.0\,\text{k}\Omega$	$+2I_3$	travel against the defined I_3

Write KVL:

$$+6 - 5I_2 + 2I_3 = 0$$

Substitute the shared current:

$$+6 - 5I_2 + 2(I_1 - I_2) = 0$$

Expand and collect:

$$+6 - 5I_2 + 2I_1 - 2I_2 = 0 \quad \Longrightarrow \quad 2I_1 - 7I_2 = -6$$

Multiply the complete equation by -1:

$$\boxed{-2I_1 + 7I_2 = 6}$$

The second matrix row is $[-2,\ 7]$ and $b_2 = 6$. Multiplying a complete equation by -1 does not change its solution.

Put both equations into one matrix

5 Align the variable order

Use the same order, $[I_1, I_2]$, in every equation and every matrix row.

$$\begin{aligned} \text{Equation 1:} \quad & 5I_1 - 2I_2 = 10 \\ \text{Equation 2:} \quad & -2I_1 + 7I_2 = 6 \end{aligned}$$

	coefficient of I_1	coefficient of I_2	right side
Equation 1	5	-2	10
Equation 2	-2	7	6

$$\underbrace{\begin{bmatrix} 5 & -2 \\ -2 & 7 \end{bmatrix}}_{A\ [\mathrm{k\Omega}]} \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_{\mathbf{x}\ [\mathrm{mA}]} = \underbrace{\begin{bmatrix} 10 \\ 6 \end{bmatrix}}_{\mathbf{b}\ [\mathrm{V}]}$$

$$[\mathrm{k\Omega}][\mathrm{mA}] = [\mathrm{V}]$$

The unit choice makes the numerical answer come out in milliamperes.

6 Use the row rule to catch transcription errors

For each row, read the matrix back as an equation before solving:

$$[5,\ -2] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = 10 \quad \Longrightarrow \quad 5I_1 - 2I_2 = 10$$

$$[-2,\ 7] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = 6 \quad \Longrightarrow \quad -2I_1 + 7I_2 = 6$$

Stumbling block: changing the variable order in only one row creates a different problem. The solver may still return a clean-looking answer.

Solve two ways and verify

7 Numerical linear algebra

Use a solver for $A\mathbf{x} = \mathbf{b}$. Do not calculate A^{-1} by hand for this task.

```
import numpy as np

A = np.array([[5.0, -2.0],
              [-2.0, 7.0]])
b = np.array([10.0, 6.0])
x = np.linalg.solve(A, b)
residual = A @ x - b
```

8 Symbolic solution

Symbolic algebra keeps exact fractions instead of decimal approximations.

```
import sympy as sp

I1, I2 = sp.symbols("I1 I2")
equations = [sp.Eq(5*I1 - 2*I2, 10),
             sp.Eq(-2*I1 + 7*I2, 6)]
exact = sp.solve(equations, (I1, I2), dict=True)[0]
```

The exact solution is

$$I_1 = \frac{82}{31}\,\text{mA}, \qquad I_2 = \frac{50}{31}\,\text{mA}, \qquad I_3 = I_1 - I_2 = \frac{32}{31}\,\text{mA}.$$

9 Verify independently

$$\text{Equation 1:}\quad 5\left(\frac{82}{31}\right) - 2\left(\frac{50}{31}\right) = 10$$

$$\text{Equation 2:}\quad -2\left(\frac{82}{31}\right) + 7\left(\frac{50}{31}\right) = 6$$

$$\text{KCL:}\quad \frac{82}{31} - \frac{50}{31} = \frac{32}{31}$$

A near-zero residual proves that the calculated currents satisfy the equations entered into Python. It does not prove that the arrows, signs, units, or original circuit model were correct.

Tomorrow's assignment

The problem: show how the completed Question 4 circuit becomes two equations, one matrix, and two matching solver results.

The essential skill: keep the shared-current definition and variable order consistent.

The challenge: explain every sign in both loop equations instead of copying the finished matrix.

The investigation: use Python help and the official NumPy or SymPy documentation when a function or object is unfamiliar.

The verification: use residuals, substitution, and $I_3 = I_1 - I_2$.

The reflection: identify the step that changed your understanding of the two loops.

Required notebook evidence

1. Write the definitions of I_1, I_2, and I_3 in a Markdown cell.
2. Show the three signed KVL terms for Loop 1 and derive Equation 1.
3. Show the three signed KVL terms for Loop 2 and derive Equation 2.
4. State the variable order and units.
5. Build A and $\mathbf{b}$, then read both matrix rows back as equations.
6. Solve with 'numpy.linalg.solve' and report the residual vector.
7. Solve the same equations with 'sympy.solve' and report exact fractions.
8. Calculate I_3 and compare all three currents with the released answer.
9. Answer the notebook reflection in complete sentences.

Progressive hints

Hint 1 - concept: the shared resistor carries $I_1 - I_2$ because the mesh currents oppose each other there.
Hint 2 - documentation: search 'numpy.linalg.solve A shape' or 'SymPy solve simultaneous equations'.
Hint 3 - technical: use rows $[5, -2]$ and $[-2, 7]$ only after you can read them back as the two standard-form equations.

Submit

Rename the notebook exactly:

`studentnumber-lastname-kirchhoff-jupyter.ipynb`

Example: `123456789-Smith-kirchhoff-jupyter.ipynb`. Keep the '.ipynb' ending. Restart the kernel, run all required cells, save, download, reopen, and submit the notebook through the assigned classroom system.

Later, not tomorrow: the intentional keyword error, array-shape error, unit bug, parameter sweep, capacitors, and RC response.